

# Ideas for On-Chip Measurement of EM Interference



by  
R. Jacob Baker  
Boise State University

# Noninvasive Ckts

---

- Must not interfere with circuit operation
- Connect to on-chip circuitry
- Robust operation (tolerant to EM interference)
- Example: Connect measuring circuit to clock distribution tree. What happens?



# **Basic idea: use a bandpass Analog-to-Digital converter employing noise-shaping**

- Output is a 1-bit word
- can be averaged to reduce (eliminate) random interference
- dynamic range can be very large
- precise analog circuitry not required







**Perhaps, most importantly,  
external clock sets center  
A/D conversion allowing  
coherent sampling (more  
on this when we discuss  
UWB measurements)**




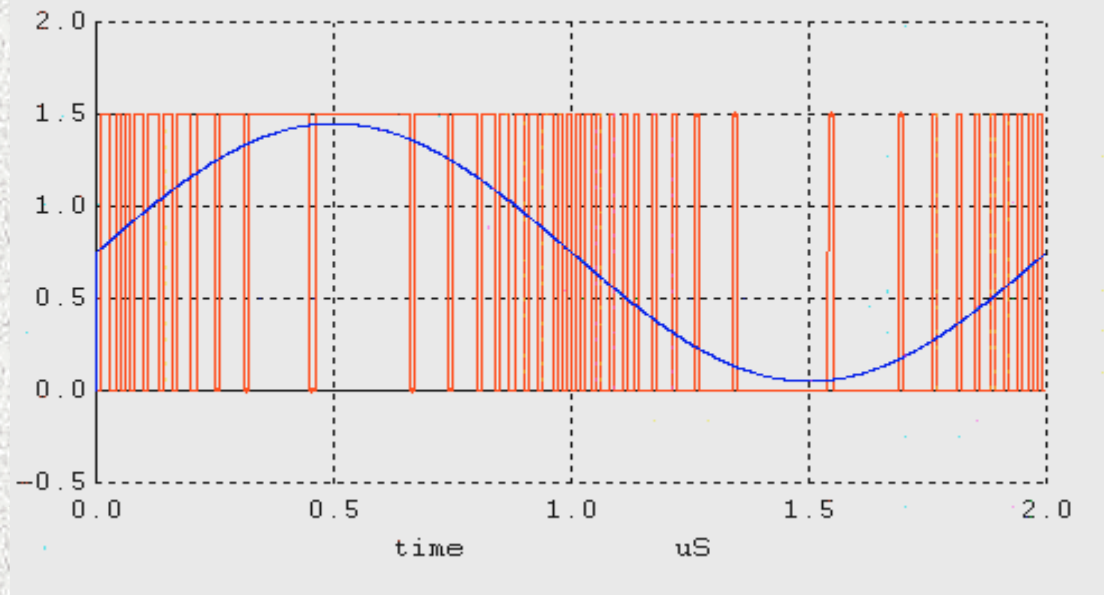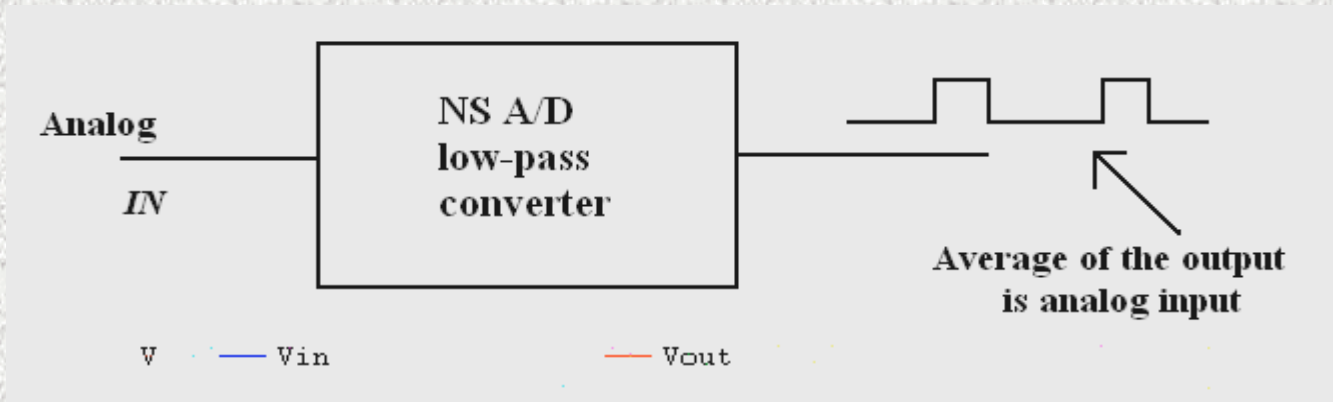
# Low Pass noise-shaping (NS) A/D conversion (a review)




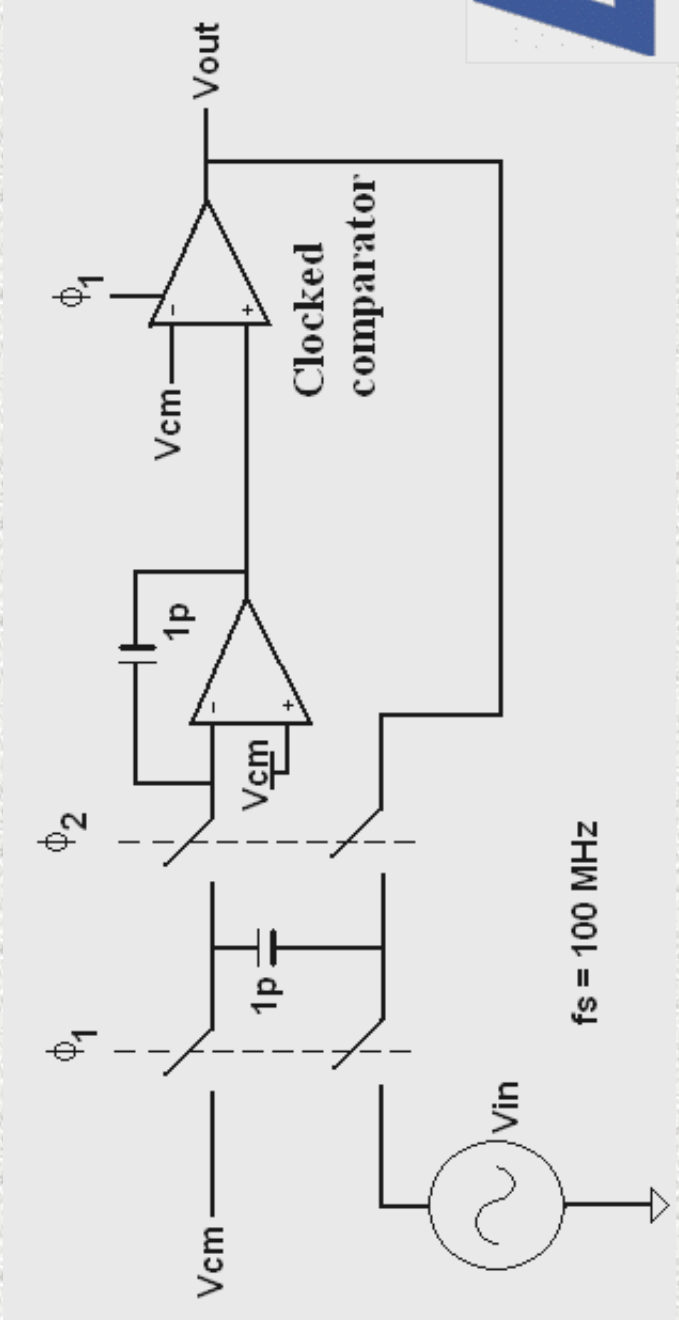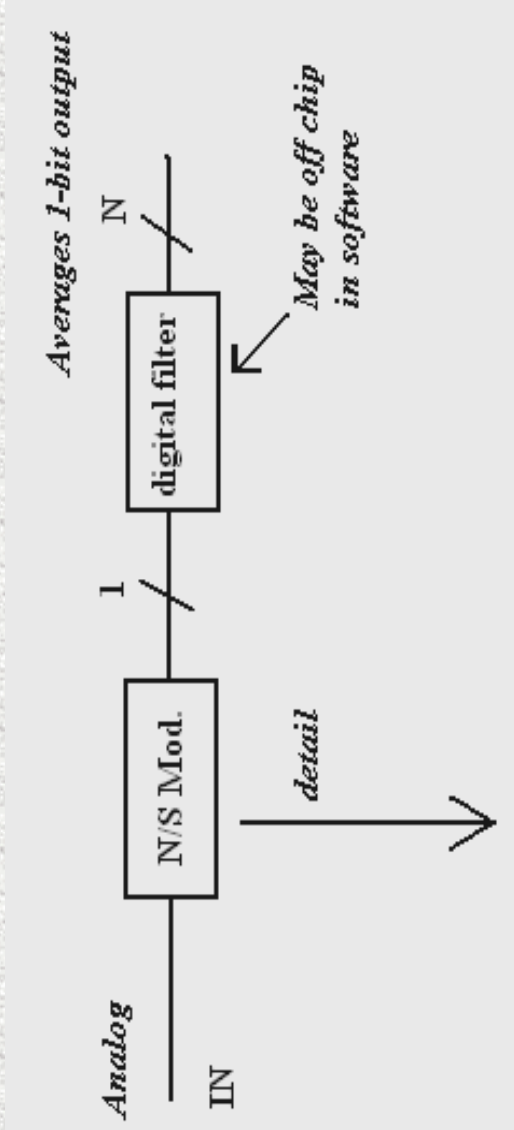



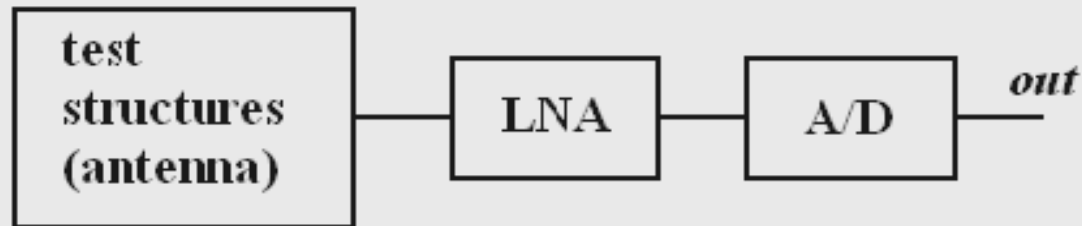
# Sensitivity can be adjusted by:

- Limiting output fed back voltage
- Inserting a LNA before A/D




# Basic circuit topology

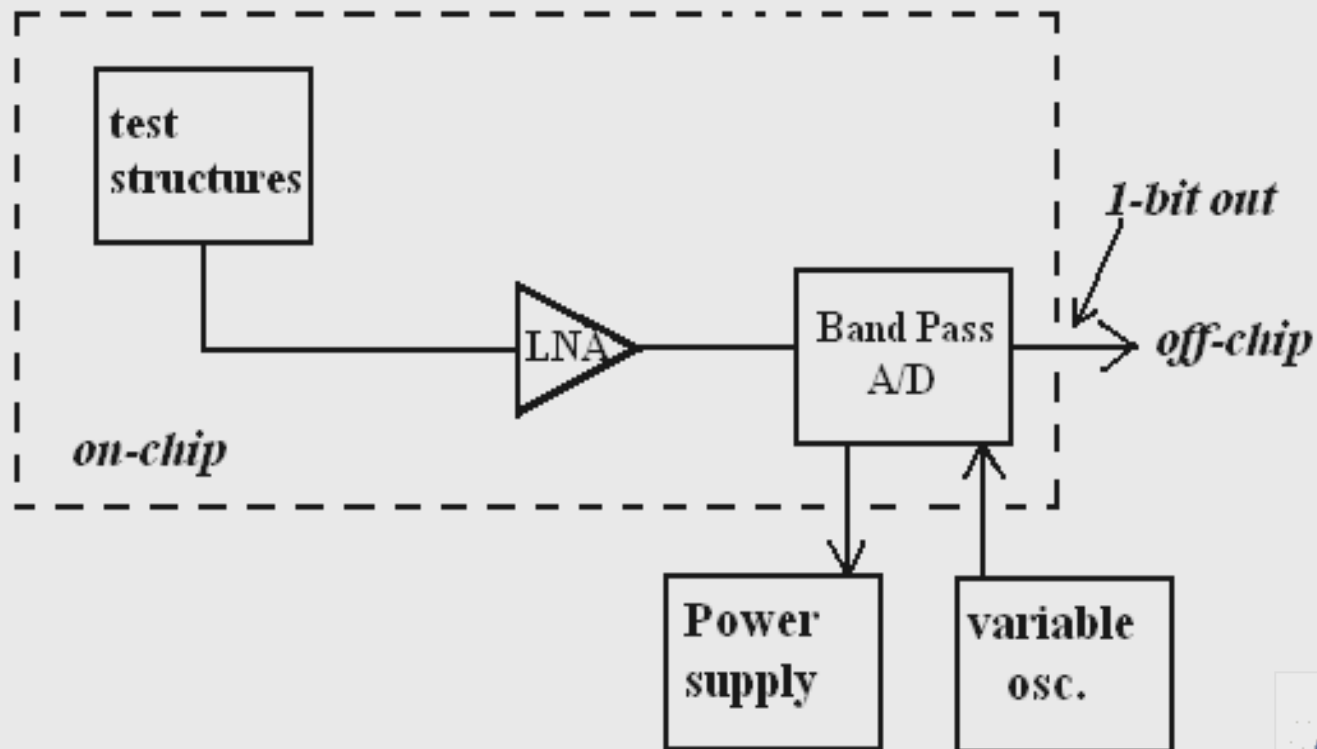




# Ultra-Wide band pulse interactions

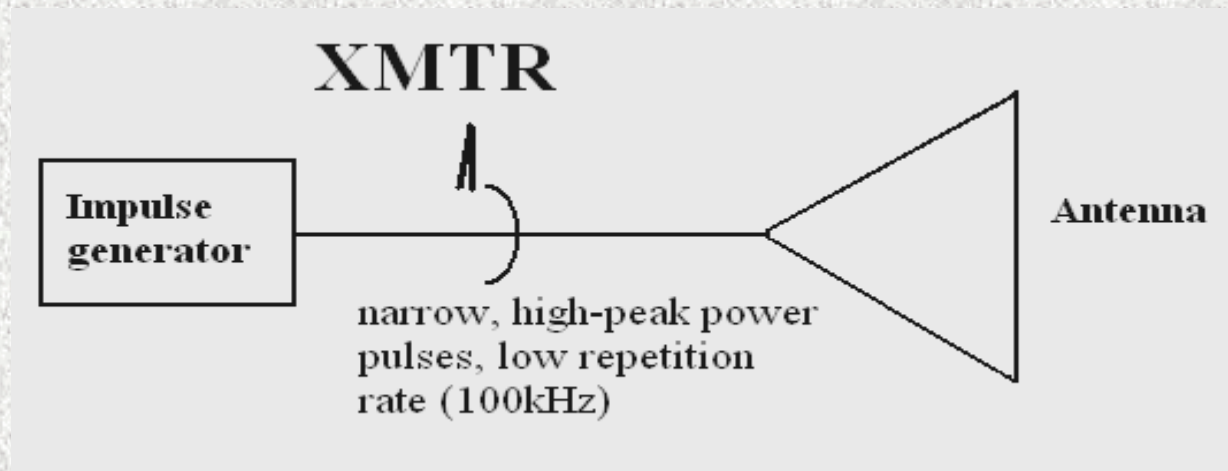

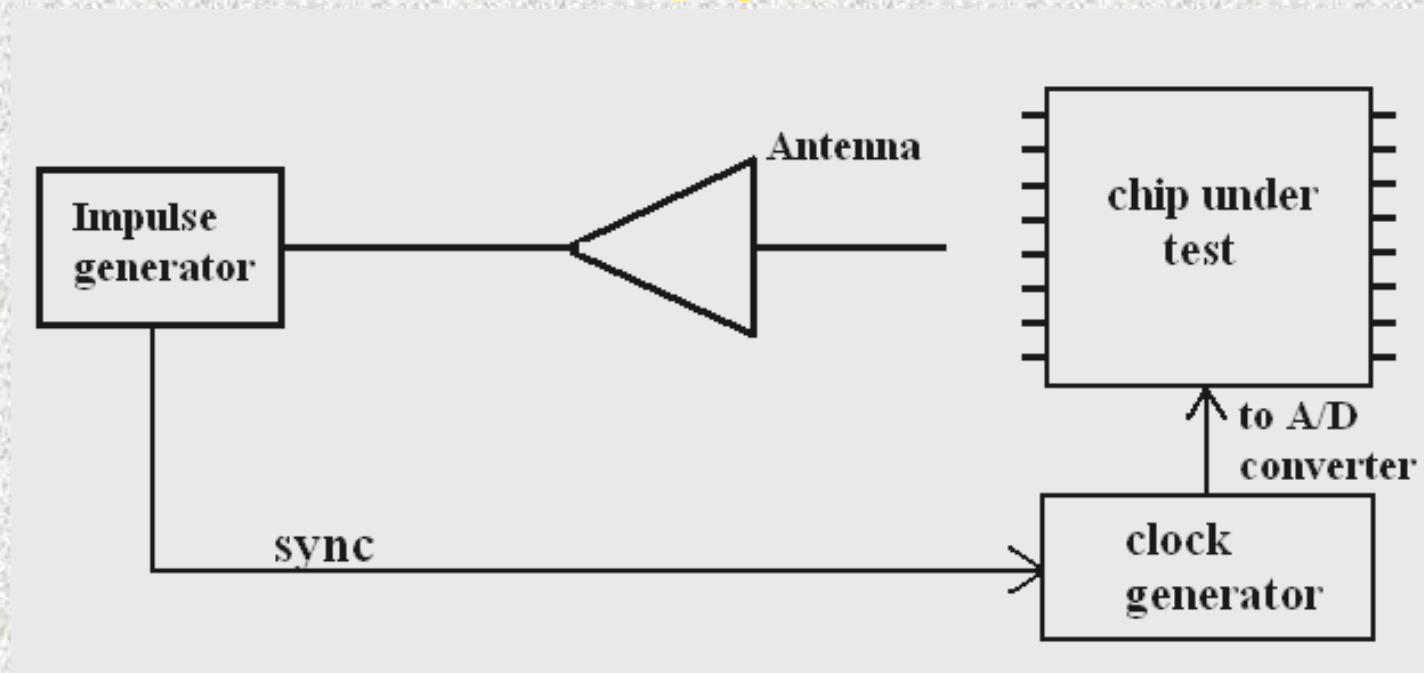- Non-invasive measurements
- Low-average power
- very difficult to detect





**Allows coherent sampling to determine UWB pulse effects**





# Summary

- Develop bandpass A/D
- Use A/D with various test structures (and LNA)
- Design oscillators (not too useful with UWB pulses)

